

# DISCOBOLUS DESIGNS

## Rethinking Signal Integrity Using Embedded Passives

Bill Gervasi

[bilge@discobolusdesigns.com](mailto:bilge@discobolusdesigns.com)

October 2014



# Agenda

History of memory signal termination

Signal integrity on flyby buses

Distributed termination for address buses


Multi-drop socketed buses

Flyby bus versus branched bus

Line conditioning for multi-drop buses




# Memory Bus Signal Termination History





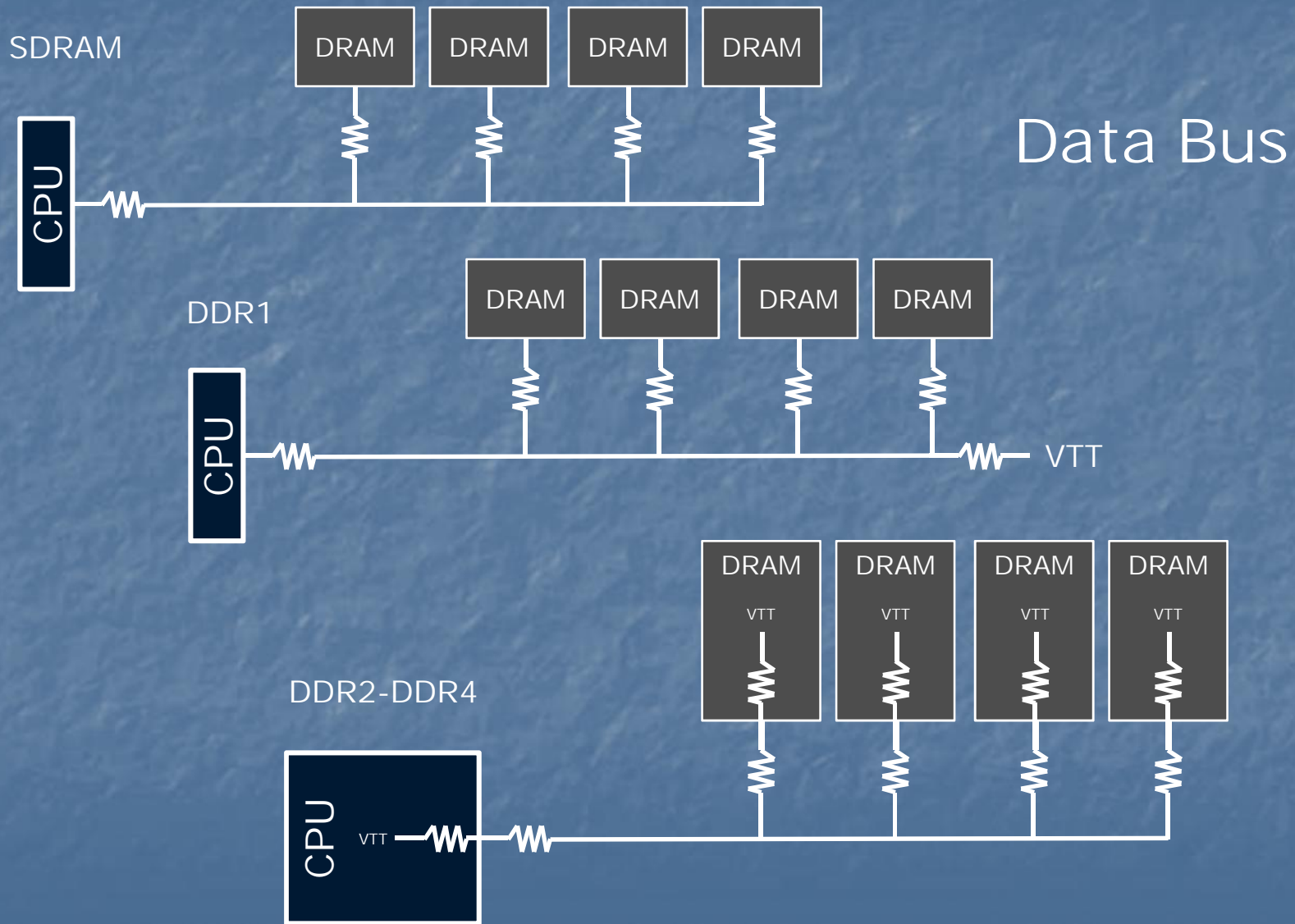




# Memory Bus Signal Termination History

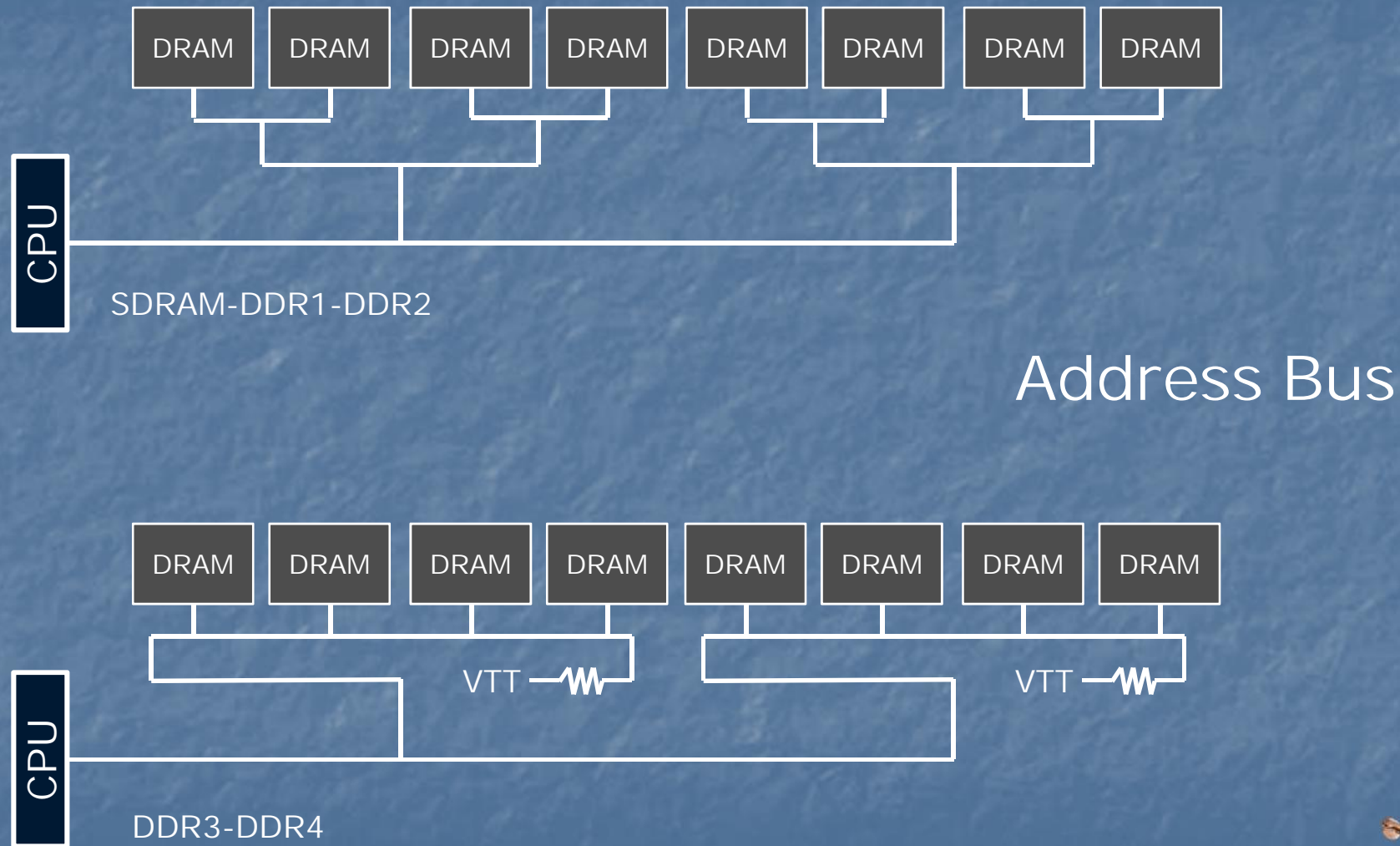


# Signal Integrity on the Fly By

  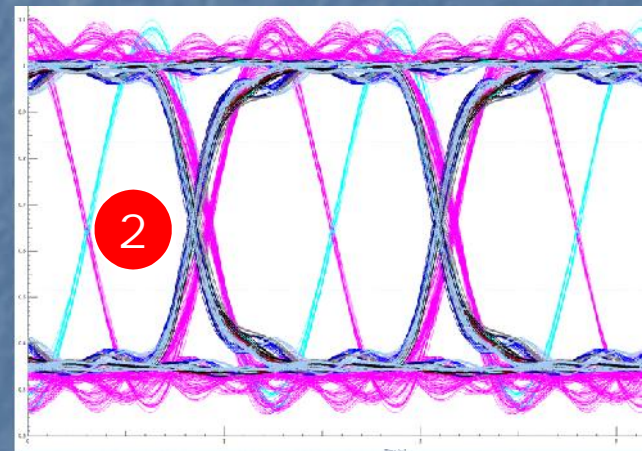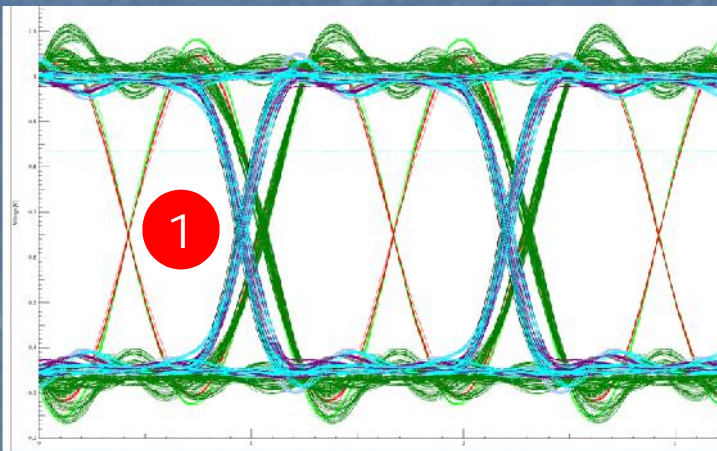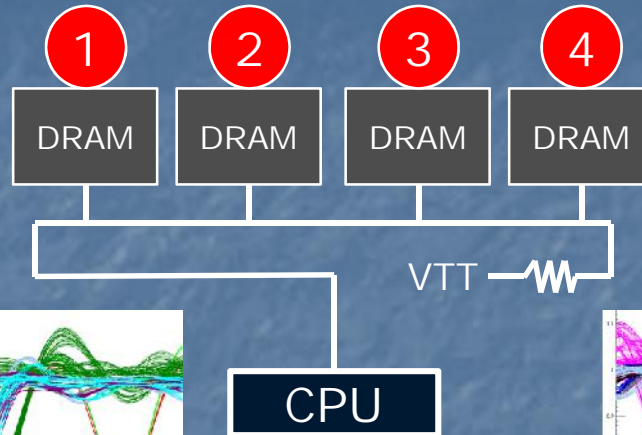




# Wishful Thinking

1  
DRAM

 


$$f_{\max} = 1136 \text{ MHz}$$

2  
DRAM

 


$$f_{\max} = 1116 \text{ MHz}$$

3  
DRAM

 

$$f_{\max} = 1089 \text{ MHz}$$

4  
DRAM

 

$$f_{\max} = 1066 \text{ MHz}$$

Solution frequency =  
 $(f_1 + f_2 + f_3 + f_4) \div 4 =$   
1101 MHz, right?


Of course not...

Solution frequency =  
 $\text{Min}(f_1 \dots f_4) =$   
1066 MHz


So how do we maximize  
signal integrity at all DRAMs?



# Distributed Address Termination

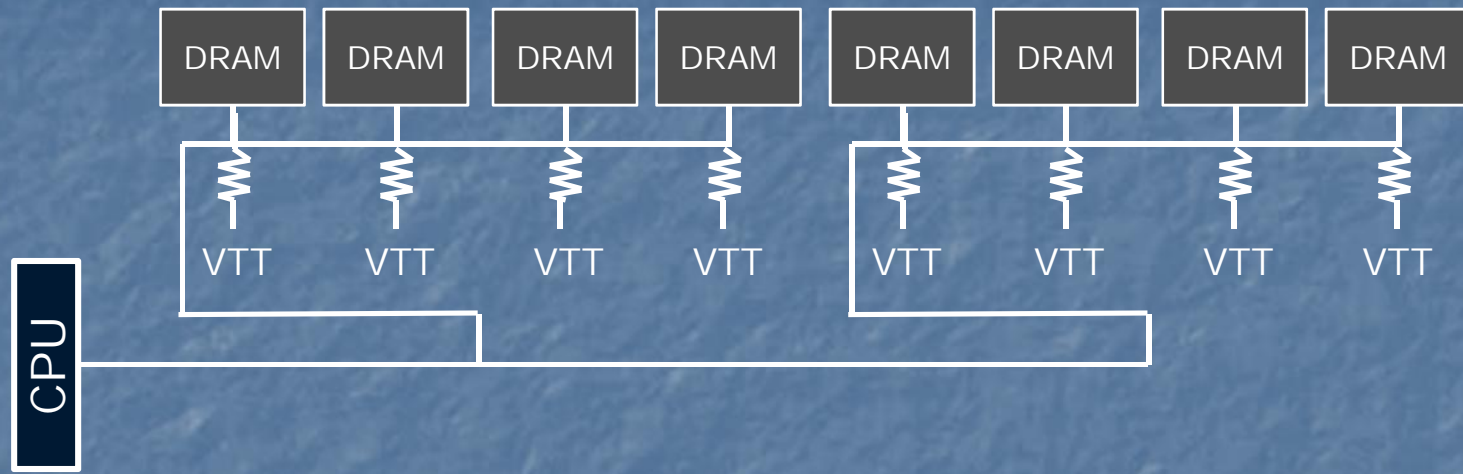

 
Problem is that termination resistors already take up 20% of available surface area



Where would we put these hundreds of resistors?



# Embedded Resistor Overview

 


Resist material  
fabbed into the PCB

Cost is the same  
whether you have  
one resistor or 1000





# Distributed Termination Using ER

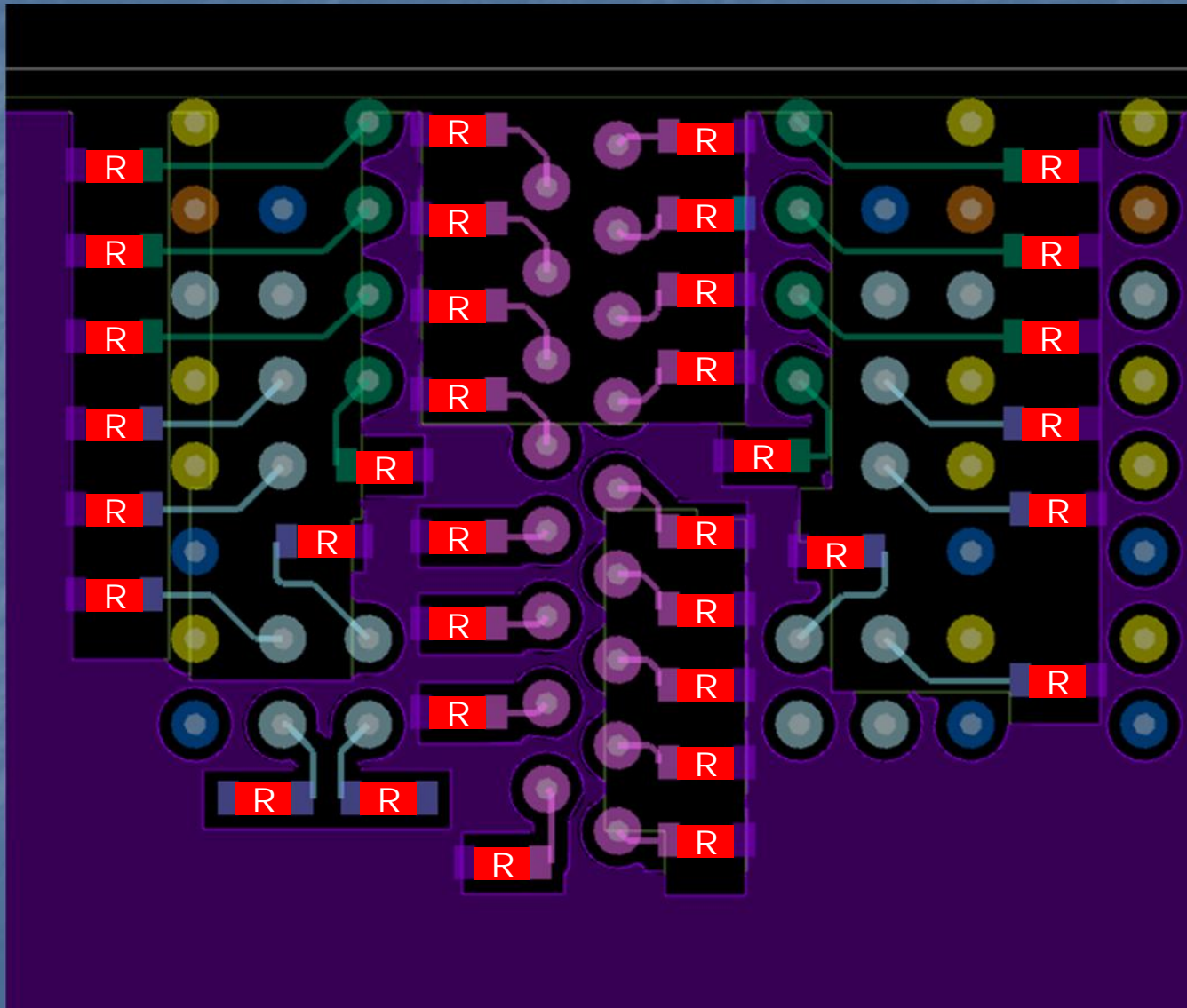


Resistance value is ratio of length to width times base resistance

$$Value = \frac{L}{W} * R$$



# Tuning Distributed Termination

 

Typical termination is 36 W

Simple distribution  $4 \times 36 = 144 \text{ W}$

Tuned distribution (eg only)


R1 = 135 W

R2 = 140 W

R3 = 149 W

R4 = 154 W

 
Still 36 W equivalent, however tuned for signal integrity at each point



Patent pending




# 3 DIMMs Per Channel

 





# Challenges in Supporting 3DPC

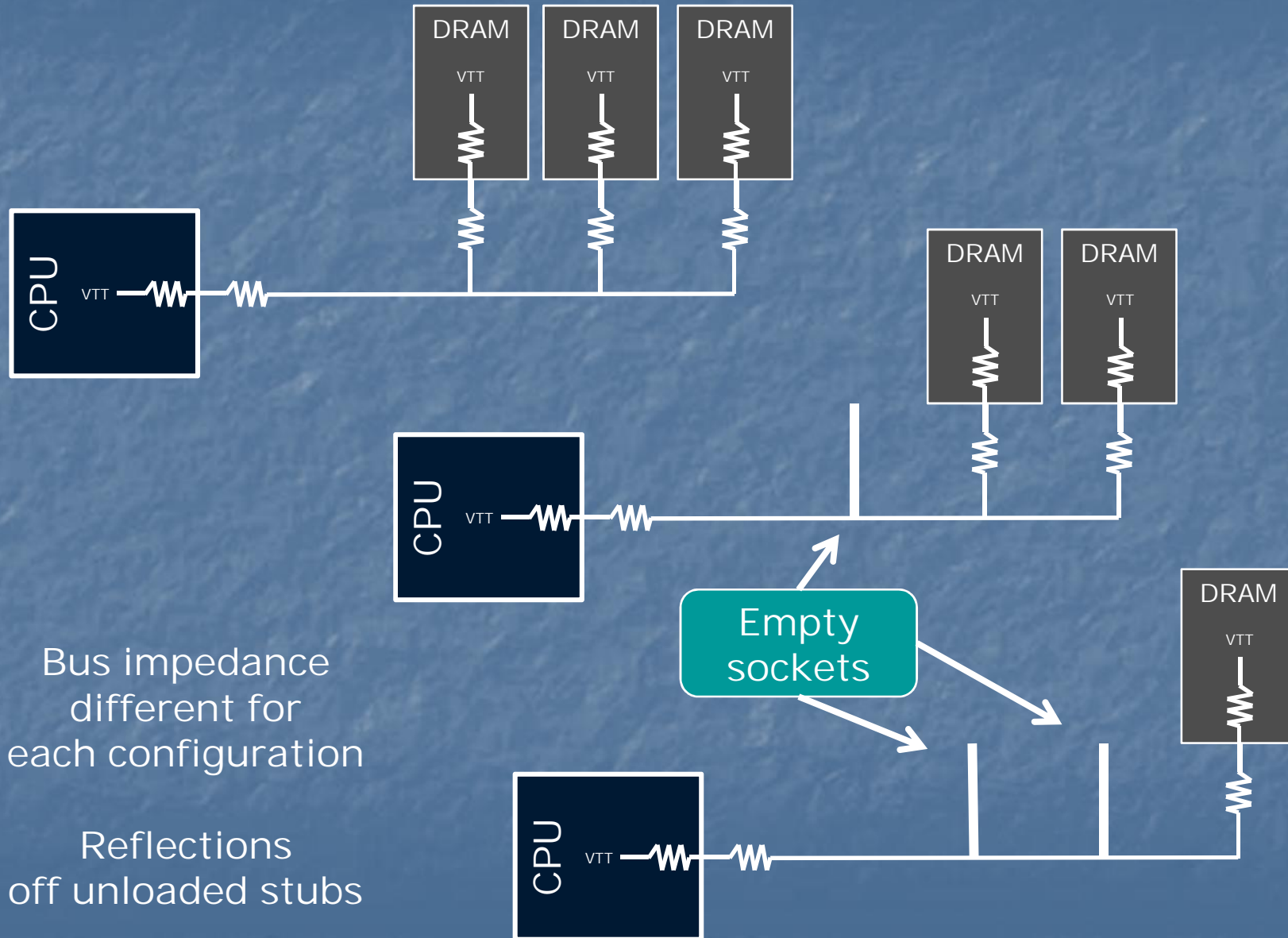

# Desirable Configuration: Branched

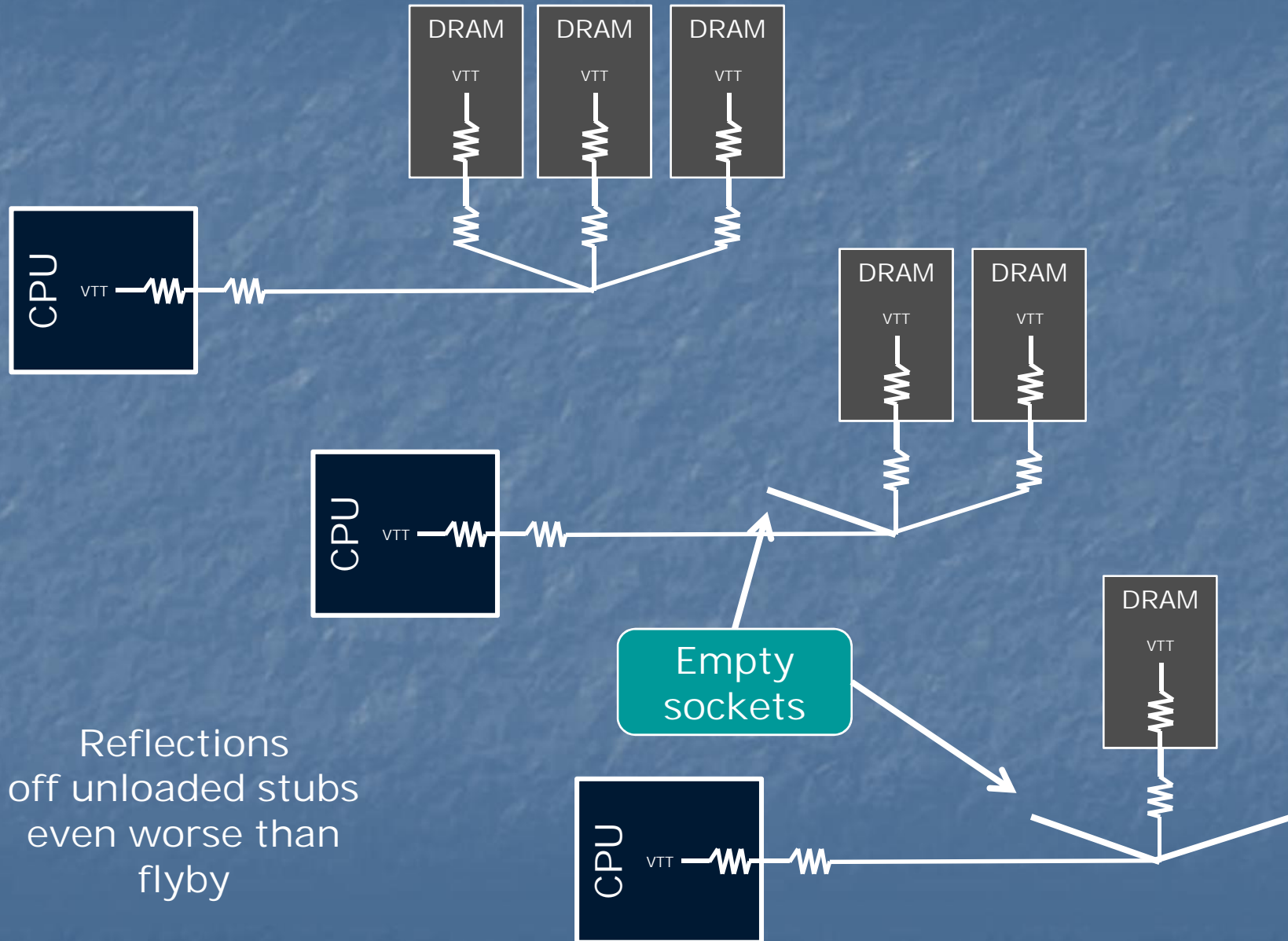

# Line Conditioning Module

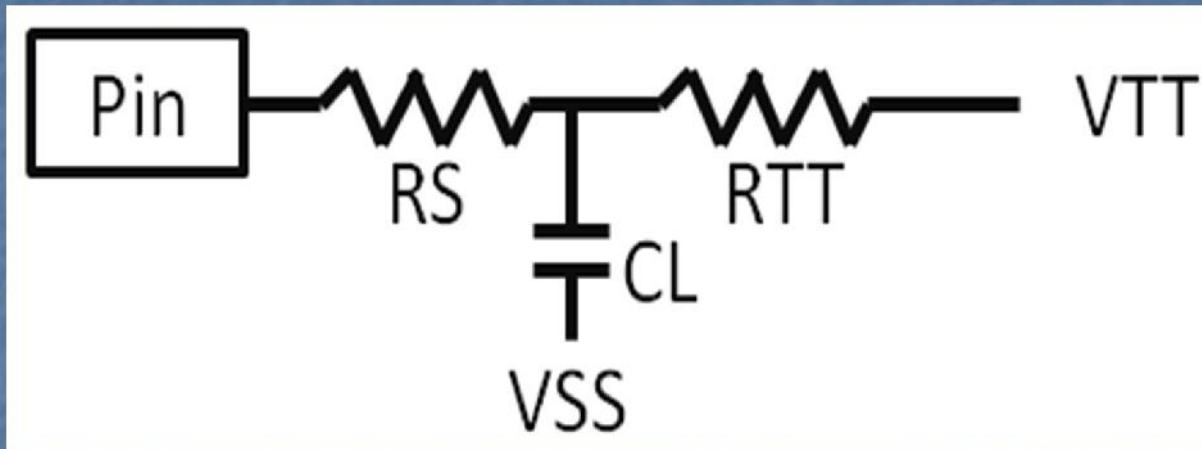

Terminates every active signal on the bus

Values match loading equivalent of 2 rank DIMM

Signal	RS	CL	RTT
Data	15 W	3.7 pF	60 W
Address	22 W	1.85 pF	100 W



DDR3 DIMM example shown






# Printed Embedded Capacitor


Ceramic epoxy suspension

  

# Termination Networks

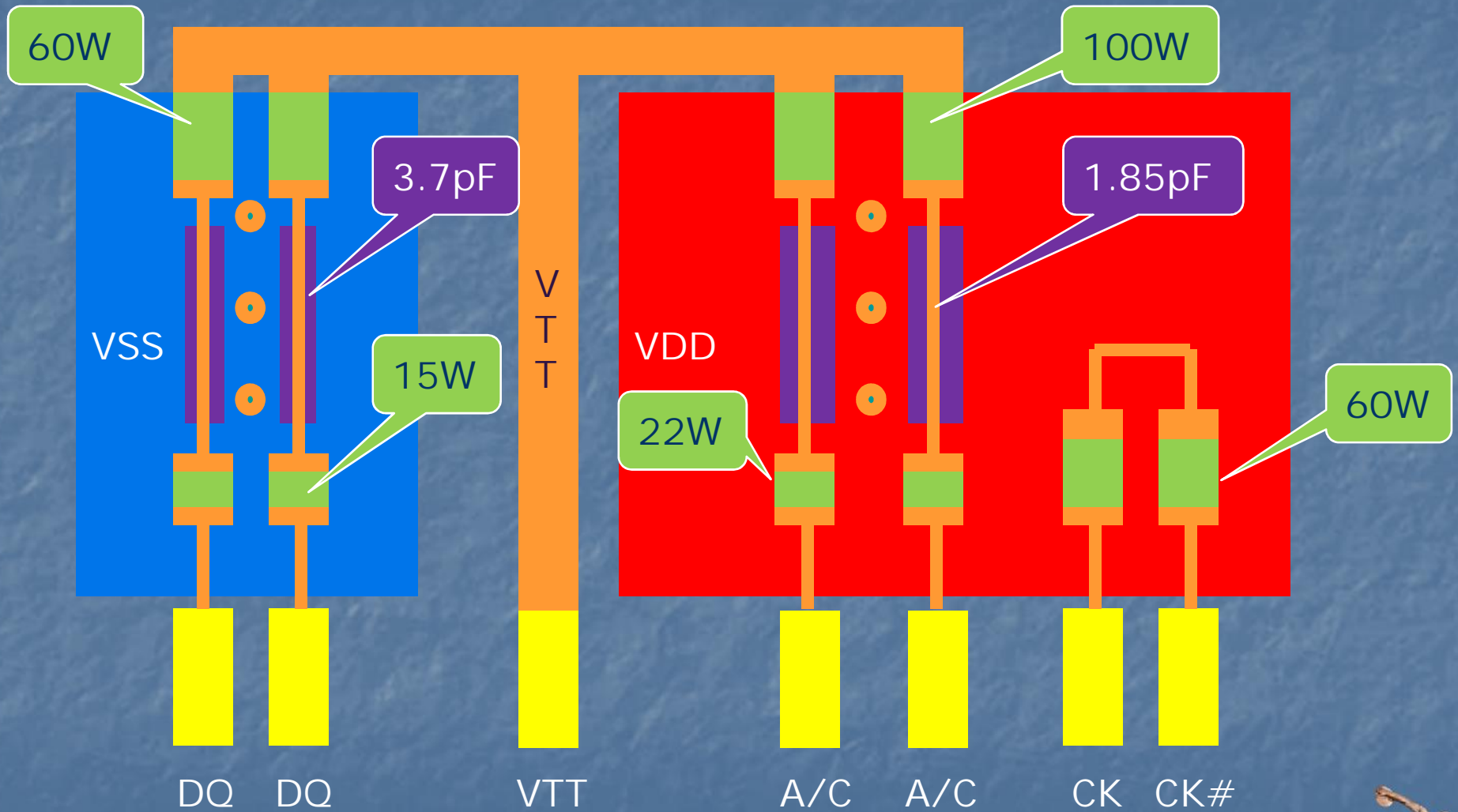

# Line Conditioning Module

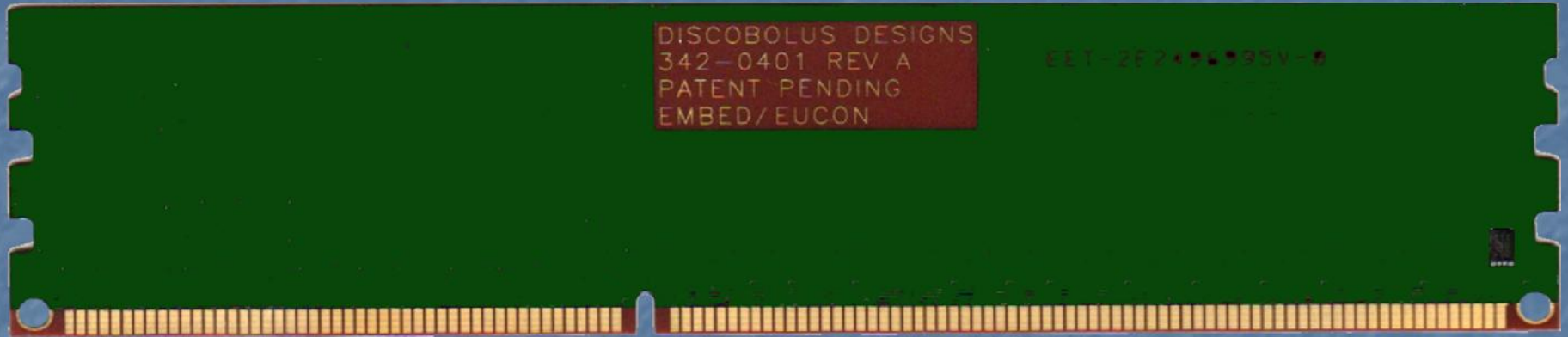

2 layer PCB

300+ Printed resistors


150+ Printed capacitors

Optional SPD: only mounted component  
can include thermal sensor





# Using Line Conditioning

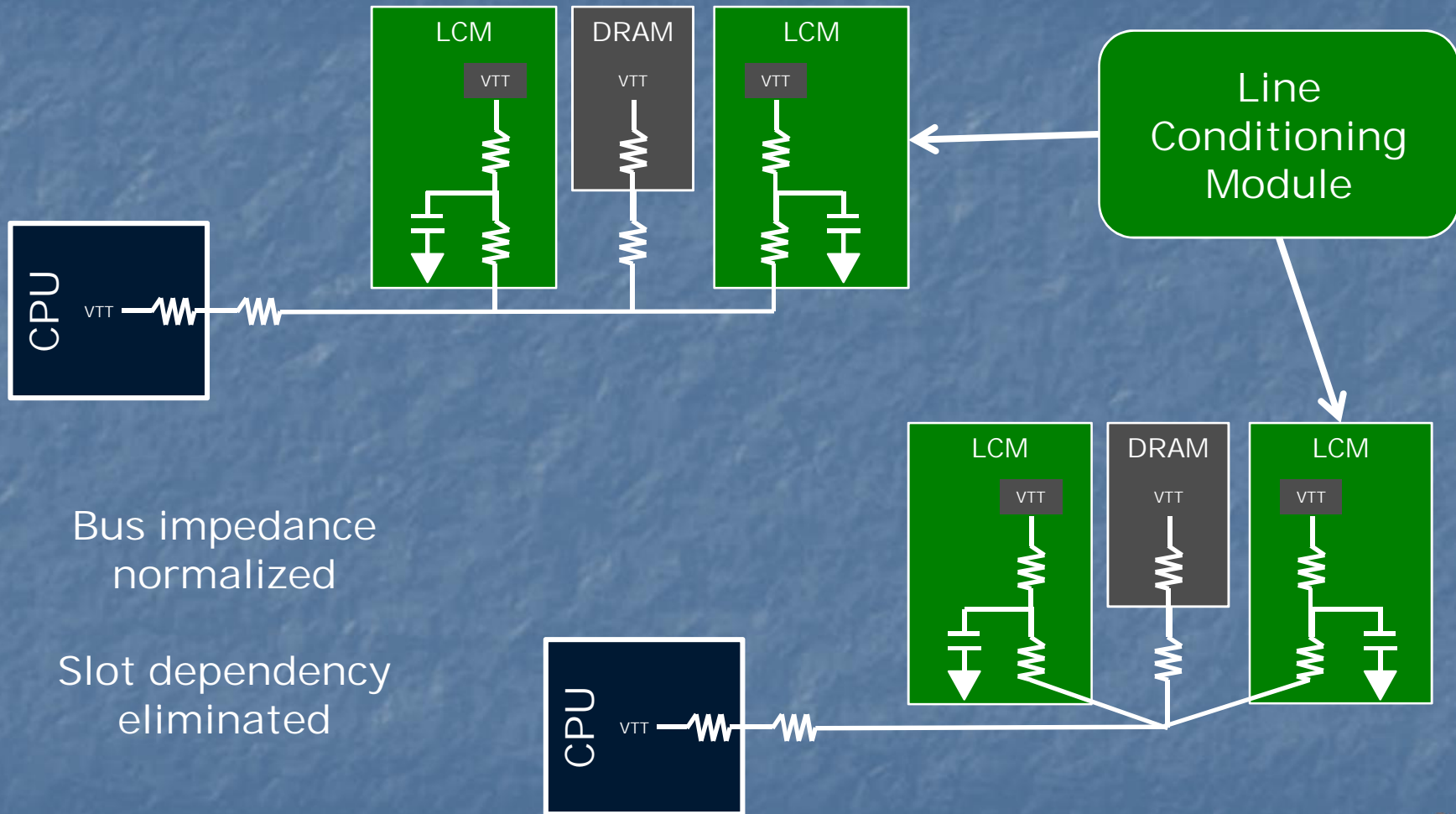


Bus impedance  
normalized

Slot dependency  
eliminated



# Nice Thermal Side Effect

 

# Concluding

Memory bus termination still evolving

Multi-drop socketed buses challenging

Embedded resistors and capacitors  
provide unique solutions to these  
problems





Thank you!

*DISCOBOLUS*  
*DESIGNS*

